



Computer Architectures

Developing a Pipeline processor

22/04/2013

**Tiago Gomes
(ESRG)**

Centro ALGORITMI
Department of Industrial Electronics
School of Engineering,
University of Minho, Guimarães - PORTUGAL





Features

- 5-Stage Pipeline
- 3-addresses Load-Store Architecture
- Data size:
 - 8-bits
- Instructions size:
 - 16-bits





Features

- Register File
 - 8 registers x 8-bits
- Instruction Memory
 - 256 x 16-bits
- Data Memory
 - 256 x 8-bits
- IO ports
 - 8-bit Input port
 - 8-bit Output port





Summary



Embedded Systems
Research Group

- Instruction Set Architecture
- Micro-Architecture
- Hazards
- Results





- Register File:
 - $RF = \{R0, R1, R2, R3, R4, R5, R6, R7\}$
- 6 Arithmetic/Logic instructions
- 4 Data transfer instructions
- 3 Control instructions





- Instructions:

- Arithmetic and logical

- ADD, SUB, AND, OR, XOR

$R_d = R_a \text{ op } R_b$

(eg., $R_3 = R_2 + R_1$)

- NOT

$R_d = \sim R_a$

(eg., $R_5 = \sim R_7$)





- Data transfer instructions
 - Immediate Load

$Rd = \text{value}$ (eg., $R3 = 0x55$)
 - Load

$Rd = \text{mem}[\text{addr}]$ (eg., $R2 = \text{mem}[3]$)
 - Store

$\text{mem}[\text{addr}] = \text{value}$ (eg., $\text{mem}[5] = R0$)
 - Input / Output

$Rd = \text{Input}$ (eg., $R5 = \text{input}$)
 $\text{Output} = Ra$ (eg., $\text{Output} = R2$)





- Control instructions

- JMP

$PC = Ra$

(eg., $PC = R1$)

- BRZ

If ($Rb == 0$) $PC = Ra$

- BRNZ

If ($Rb \neq 0$) $PC = Ra$

- Miscellaneous

- NOP

($PC = PC + 1$)





Summary

- Microprocessor ISA definition
- **Micro-Architecture**
- Hazards
- Results





- First step: instruction encoding
 - Our ISA specifies 13 instructions
 - How many bits for the opcode?
 - How many bits to address the Register File?
 - ...
 - How can an ALU instruction be encoded?

ADD Rd, Ra, Rb





- ADD instruction

add Rd, Ra, Rb

opcode	Rd	Ra	Rb			
1 1 0 0	b b b	b b b	b b b	x	x	x

$Rd = Ra + Rb$

- Other ALU instructions

add Rd, Ra, Rb
sub Rd, Ra, Rb
and Rd, Ra, Rb
or Rd, Ra, Rb
xor Rd, Ra, Rb
not Rd, Ra

opcode	Rd	Ra	Rb			
1 1 0 0	b b b	b b b	b b b	x	x	x
0 0 0 1	b b b	b b b	b b b	x	x	x
0 0 1 0	b b b	b b b	b b b	x	x	x
0 0 1 1	b b b	b b b	b b b	x	x	x
0 1 0 0	b b b	b b b	b b b	x	x	x
0 1 0 1	b b b	b b b	x x x	x	x	x

$Rd = Ra + Rb$

$Rd = Ra - Rb$

$Rd = Ra \& Rb$

$Rd = Ra | Rb$

$Rd = Ra \wedge Rb$

$Rd = \sim Ra$





• Load and Store

loadi Rd, imm

opcode	Rd		immediate
0 1 1 0	b b b	x	b b b b b b b b

Rd = imm

load Rd, @Rb

opcode	Rd		Rb		i
0 1 1 1	b b b	x x x	b b b	x x	0

Rd = mem[Rb]

store Ra, @Rb

opcode		Ra	Rb		i
1 0 0 0	x x x	b b b	b b b	x x	0

mem[Rb] = Ra

load Rd, imm

opcode	Rd	immediate	i
0 1 1 1	b b b	b b b b b b b b	1

Rd = mem[imm]

store Ra, imm

opcode	Imm [7:5]	Ra	imm[4:0]	i
1 0 0 0	b b b	b b b	b b b b b	1

mem[imm] = Ra





• Other instructions

input Rd
output Ra

opcode	Rd	Ra		i
1 1 0 1	b b b	x x x	x x x x x	0
1 1 0 1	x x x	b b b	x x x x x	1

Rd = input
output = Ra

jmp @Ra

opcode	Rd	Ra	
1 0 0 1	x x x	b b b	x x x x x x

PC = Ra

brz Rb, @Ra
brnz Rb, @Ra

opcode	Rd	Ra	Rb	
1 0 1 0	x x x	b b b	b b b	x x x
1 0 1 1	x x x	b b b	b b b	x x x

if(Rb==0) PC = Ra
if(Rb≠0) PC = Ra

nop

opcode	
0 0 0 0	x x x x x x x x x x x x





Pipeline

- Is it possible to divide instructions in several tasks/stages?
 - **Fetch & Decode Stages**
 - Read instruction from memory and decode it
 - **Execute Stage**
 - Perform the calculations (ALU)
 - **Memory Access Stage**
 - Read or Write to Data Memory
 - **Write-Back**
 - Write back the result to the Register File






Pipeline




Embedded Systems
Research Group

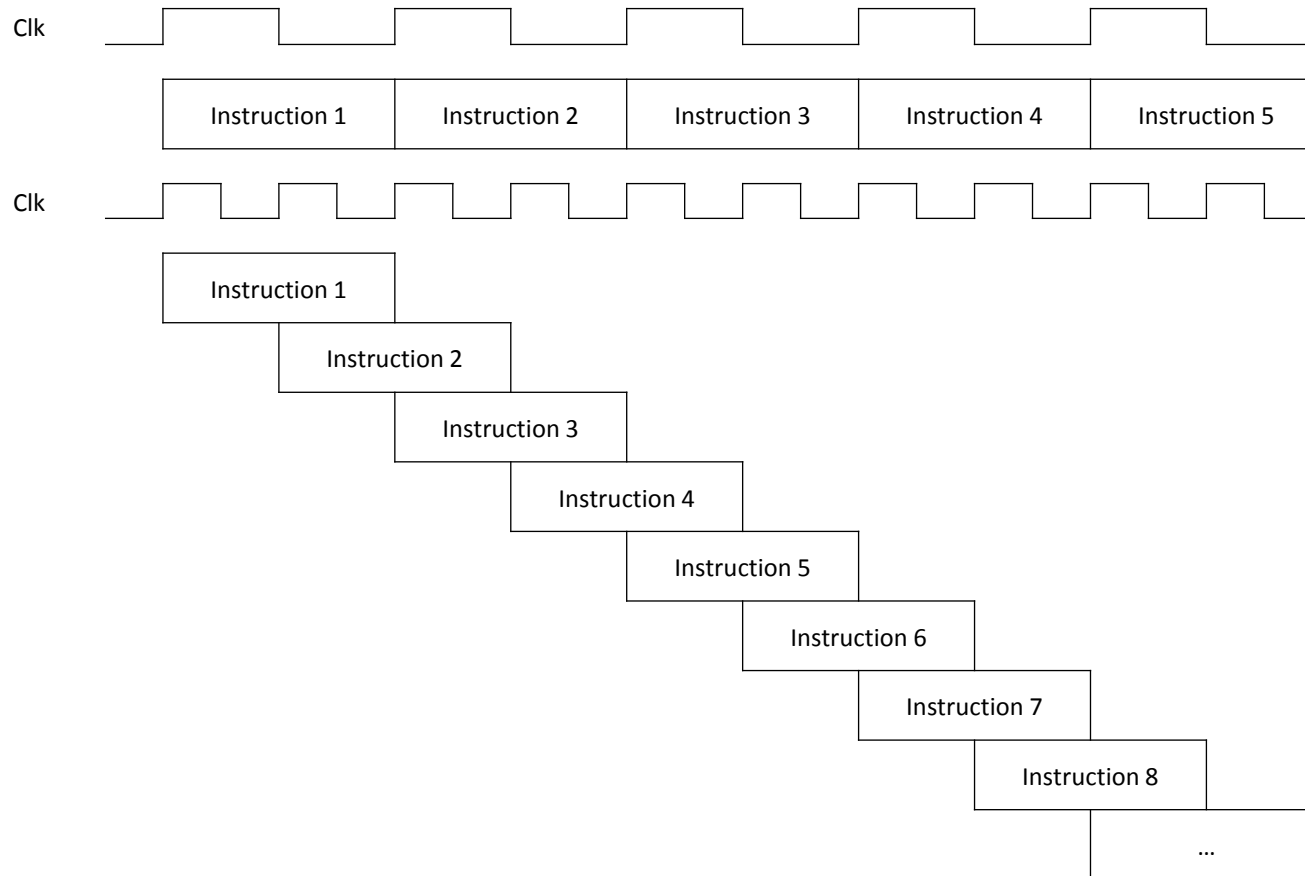



Pipeline


• Pipeline

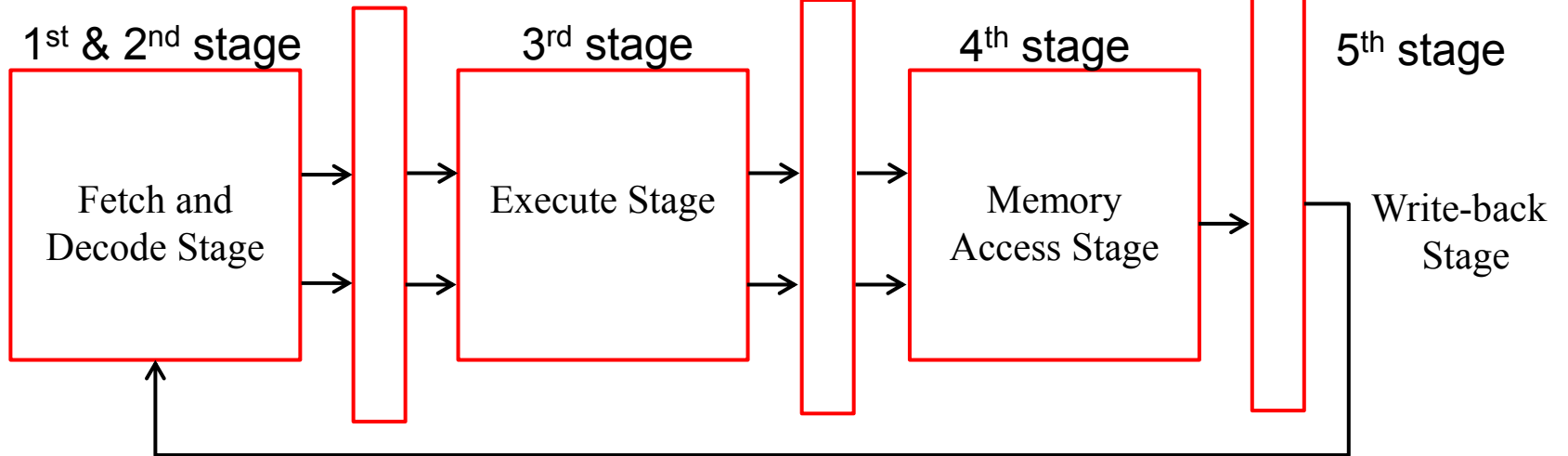



Pipeline

- ALU instruction by stages

 




Pipeline

- Add Rd, Ra, Rb

- 1st & 2nd stages:

- Fetch instruction and Read Operands

 

add Rd, Ra, Rb

opcode	Rd	Ra	Rb			
1 1 0 0	b b b	b b b	b b b	x	x	x




Pipeline

- Add Rd, Ra, Rb

- 3rd stage:

- Calculation

 

add Rd, Ra, Rb

opcode	Rd	Ra	Rb			
1 1 0 0	b b b	b b b	b b b	x	x	x




Pipeline

- Add Rd, Ra, Rb

- 4th stage:

- Do nothing

 


add Rd, Ra, Rb

opcode	Rd	Ra	Rb			
1 1 0 0	b b b	b b b	b b b	x	x	x



Pipeline

 - Add Rd, Ra, Rb
 - 5th stage:
 - Write-back the result



add Rd, Ra, Rb

opcode	Rd	Ra	Rb			
1 1 0 0	b b b	b b b	b b b	x	x	x




Pipeline

- Loadi Rd, value

- 1st & 2nd stages:

- Fetch instruction and Read Operands

 


loadi Rd, imm

opcode	Rd		immediate
0 1 1 0	b b b	x	b b b b b b b b



- Loadi Rd, value

- 3rd stage:

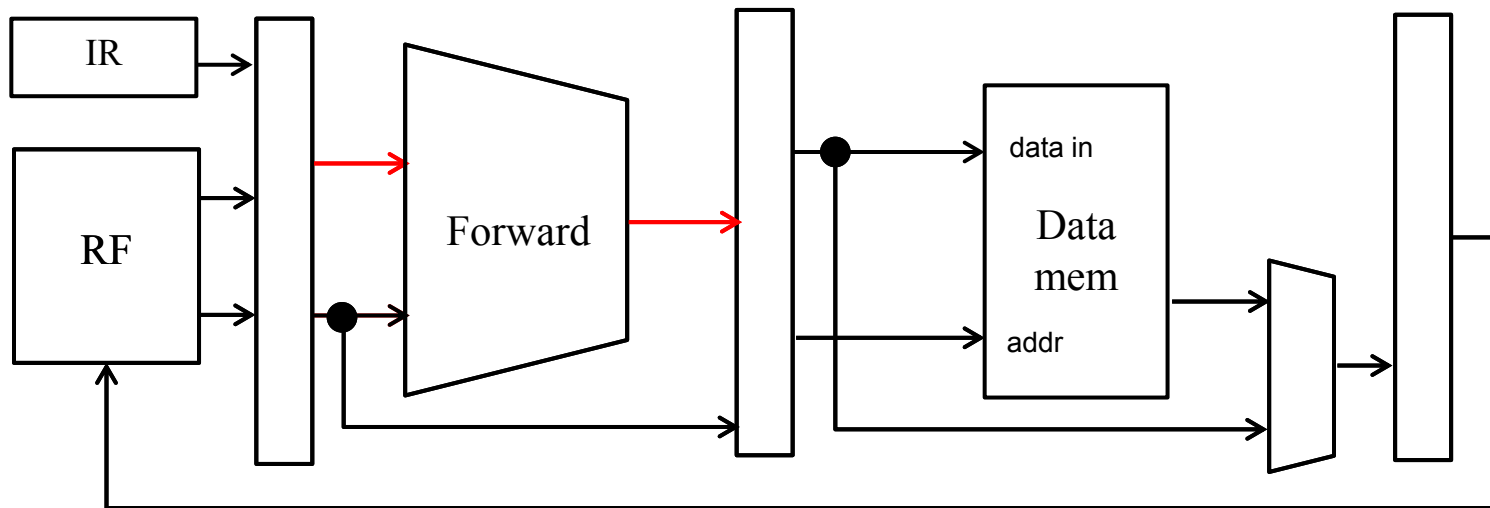


loadi Rd, imm

opcode	Rd		immediate
0 1 1 0	b b b	x	b b b b b b b b



- Loadi Rd, value

- 4th stage:

 

loadi Rd, imm


opcode	Rd		immediate
0 1 1 0	b b b	x	b b b b b b b b



- Loadi Rd, value

- 5th stage:

- Write-back the result

 

loadi Rd, imm


opcode	Rd		immediate
0 1 1 0	b b b	x	b b b b b b b b



- Store Ra, @Rb ($\text{mem}[\text{Rb}] = \text{Ra}$)

- 1st & 2nd stages:

- Fetch instruction and Read Operands

 

store Ra, @Rb

opcode		Ra	Rb		i
1 0 0 0	x x x	b b b	b b b	x x	0




-
- The diagram illustrates a processor architecture with the following components and data flow:
- IR (Instruction Register)** and **RF (Register File)** provide inputs to a vertical bar (multiplexer).
 - The vertical bar has two outputs: a red line going to the **Forward** block and a black line going to a second vertical bar.
 - The **Forward** block (a trapezoid) receives the red line and has a red output line going to the second vertical bar.
 - The second vertical bar has two outputs: a black line going to the **Data mem** block and a black line going to a third vertical bar.
 - The **Data mem** block (Data Memory) has inputs for **data in** and **addr**. It receives the black line from the second vertical bar as **data in** and the black line from the first vertical bar as **addr**.
 - The **Data mem** block has an output going to a fourth vertical bar.
 - The fourth vertical bar has an output going to a final vertical bar on the right.
 - A feedback loop exists from the final output back to the **RF** block.

opcode		Ra	Rb		i
1 0 0 0	x x x	b b b	b b b	x x	0



- Store Ra, @Rb ($\text{mem}[\text{Rb}] = \text{Ra}$)

- 4th stage:

 

store Ra, @Rb


opcode		Ra	Rb		i
1 0 0 0	x x x	b b b	b b b	x x	0



- Store Ra, @Rb ($\text{mem}[\text{Rb}] = \text{Ra}$)

- 5th stage:

- Do nothing

 


store Ra, @Rb

opcode		Ra	Rb		i
1 0 0 0	x x x	b b b	b b b	x x	0



- Read Input pins

 


input Rd



- Input Rd (Rd = Input)

- 5th stage:

- Write-back result

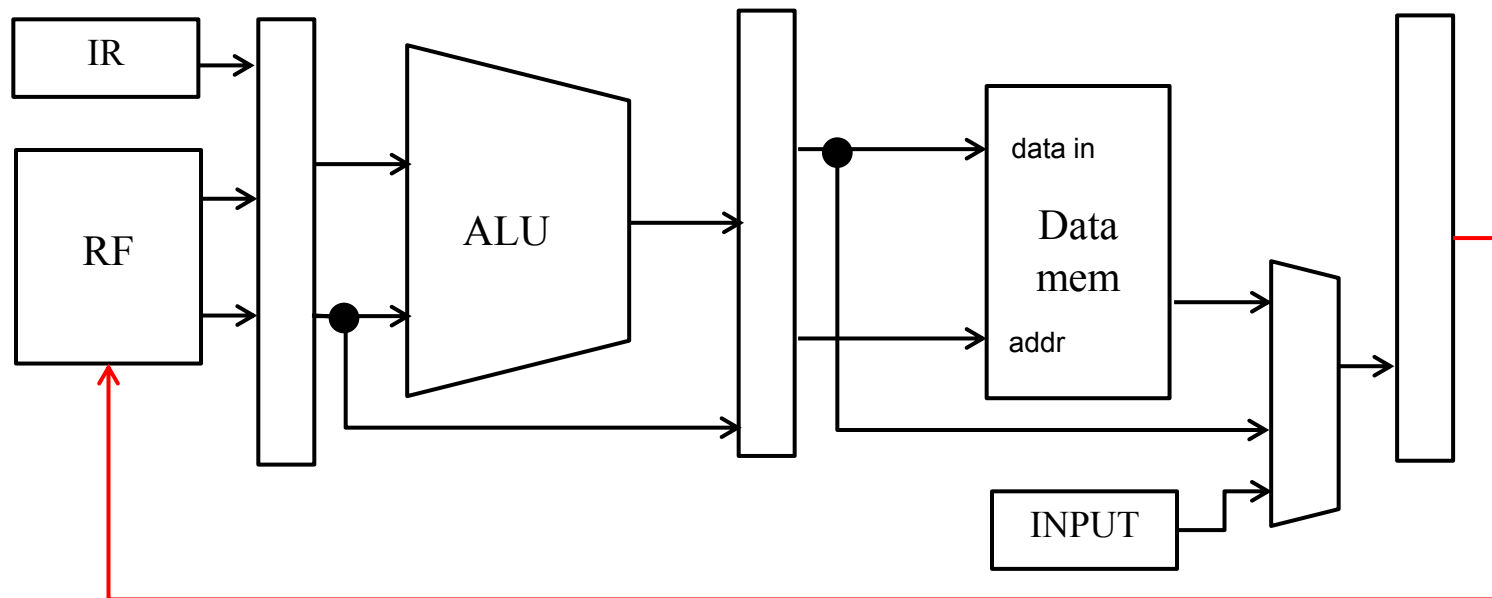

input Rd

opcode	Rd	Ra		i
1 1 0 1	b b b	x x x	x x x x x	0



Hazards



Embedded Systems
Research Group

- Data Hazards
- Control Hazards
- Structural Hazards





- Let's run this code

0	input	R0	(R0 = input = 1)
1	loadi	R2, 8	(R2 = 8)
2	loadi	R6, 0	(R6 = 0)
3	loadi	R7, 50	(R7 = 50)
4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)
6	store	R1, @R7	(mem[50] = 6)
7	load	R5, @R7	(R5 = mem[50] = 6)
8	sub	R5, R5, R0	(R5 = R5 - 1)
9	brnz	R5, @R2	(if(R5!=0) PC = 8)
10	loadi	R3, 255	(R3 = 255)
11	output	R3	(output = 255)





• Hazards?

0	input	R0	(R0 = input = 1)
1	loadi	R2, 8	(R2 = 8)
2	loadi	R6, 0	(R6 = 0)
3	loadi	R7, 50	(R7 = 50)
4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)
6	store	R1, @R7	(mem[50] = 6)
7	load	R5, @R7	(R5 = mem[50] = 6)
8	sub	R5, R5, R0	(R5 = R5 - 1)
9	brnz	R5, @R2	(if (R5 != 0) PC = 8)
10	loadi	R3, 255	(R3 = 255)
11	output	R3	(output = 255)





• Hazards?

0	input	R0	(R0 = input = 1)
1	loadi	R2, 8	(R2 = 8)
2	loadi	R6, 0	(R6 = 0)
3	loadi	R7, 50	(R7 = 50)
4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)
6	store	R1, @R7	(mem[50] = 6)
7	load	R5, @R7	(R5 = mem[50] = 6)
8	sub	R5, R5, R0	(R5 = R5 - 1)
9	brnz	R5, @R2	(if (R5 != 0) PC = 8)
10	loadi	R3, 255	(R3 = 255)
11	output	R3	(output = 255)

Data Hazard





- How to solve this hazard?

0	input	R0	(R0 = input = 1)
1	loadi	R2, 8	(R2 = 8)
2	loadi	R6, 0	(R6 = 0)
3	loadi	R7, 50	(R7 = 50)
4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)
6	store	R1, @R7	(mem[50] = 6)
7	load	R5, @R7	(R5 = mem[50] = 6)
8	sub	R5, R5, R0	(R5 = R5 - 1)
9	brnz	R5, @R2	(if (R5 != 0) PC = 8)
10	loadi	R3, 255	(R3 = 255)
11	output	R3	(output = 255)


Data Hazard





• First solution: Using NOPs

4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)

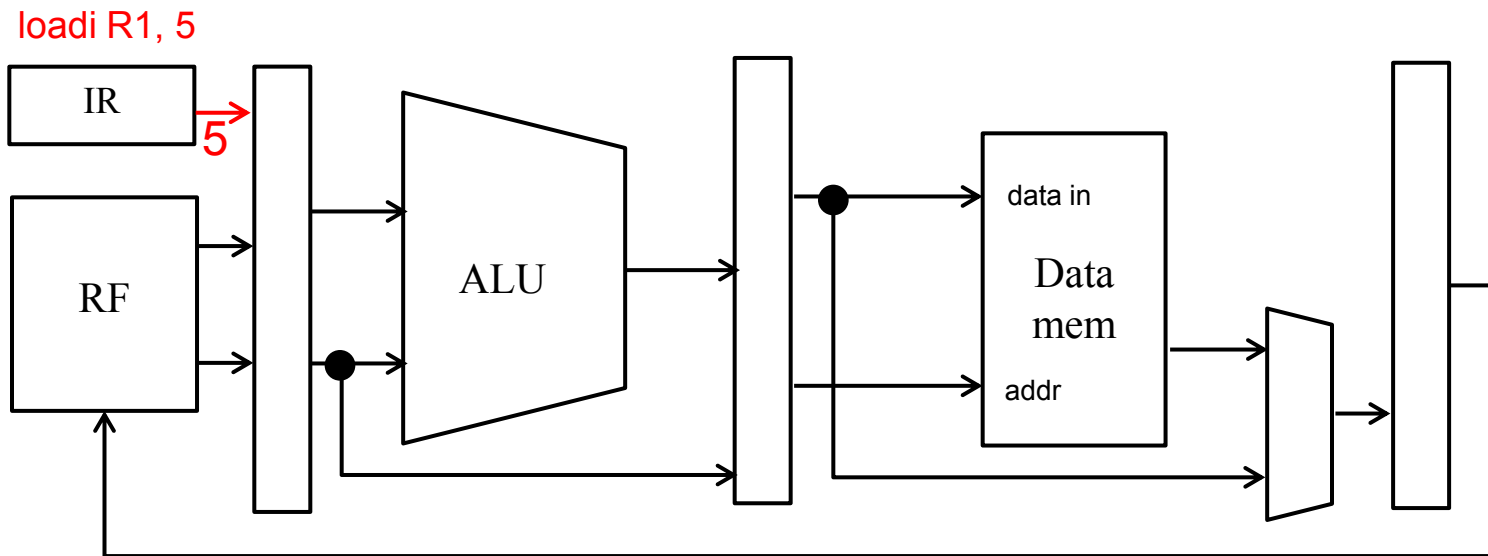 Data Hazard

loadi Rd, imm


opcode	Rd		immediate
0 1 1 0	b b b	x	b b b b b b b b



- First solution: Using NOPs

4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)


Data Hazard

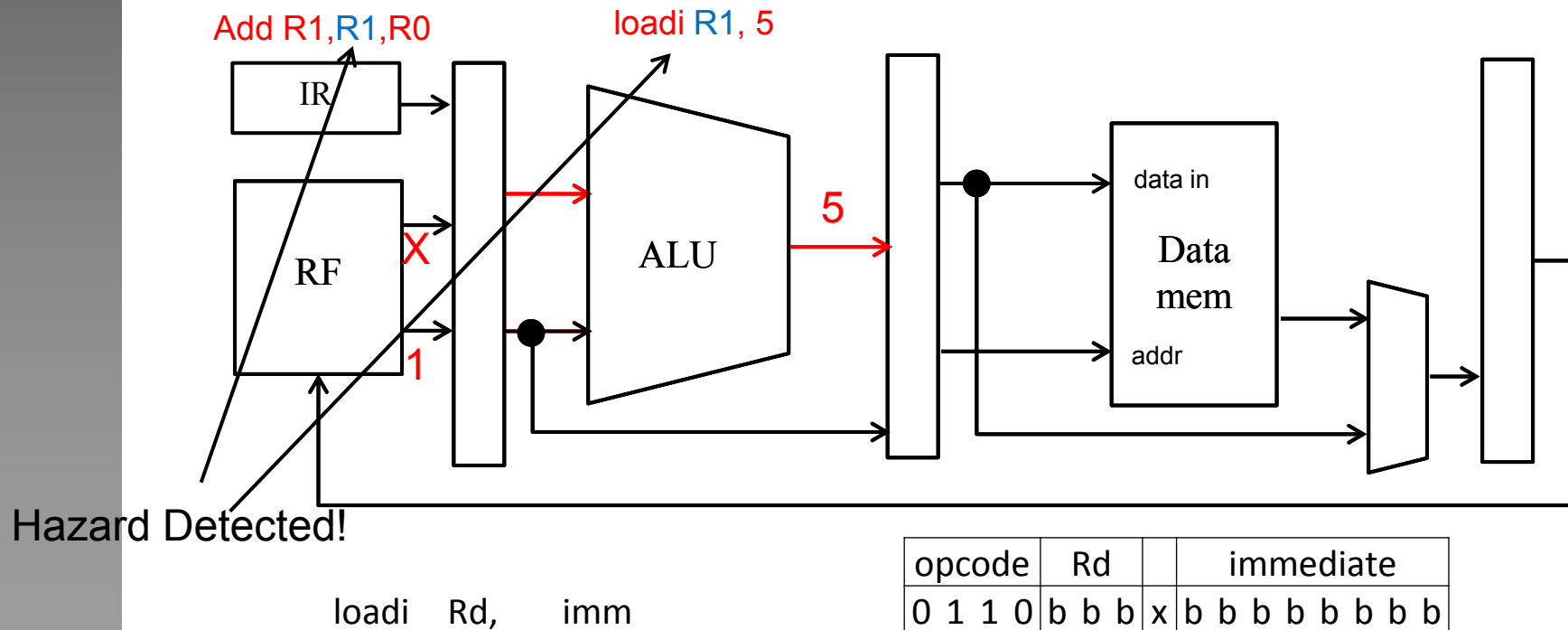



• First solution: Using NOPs

4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)

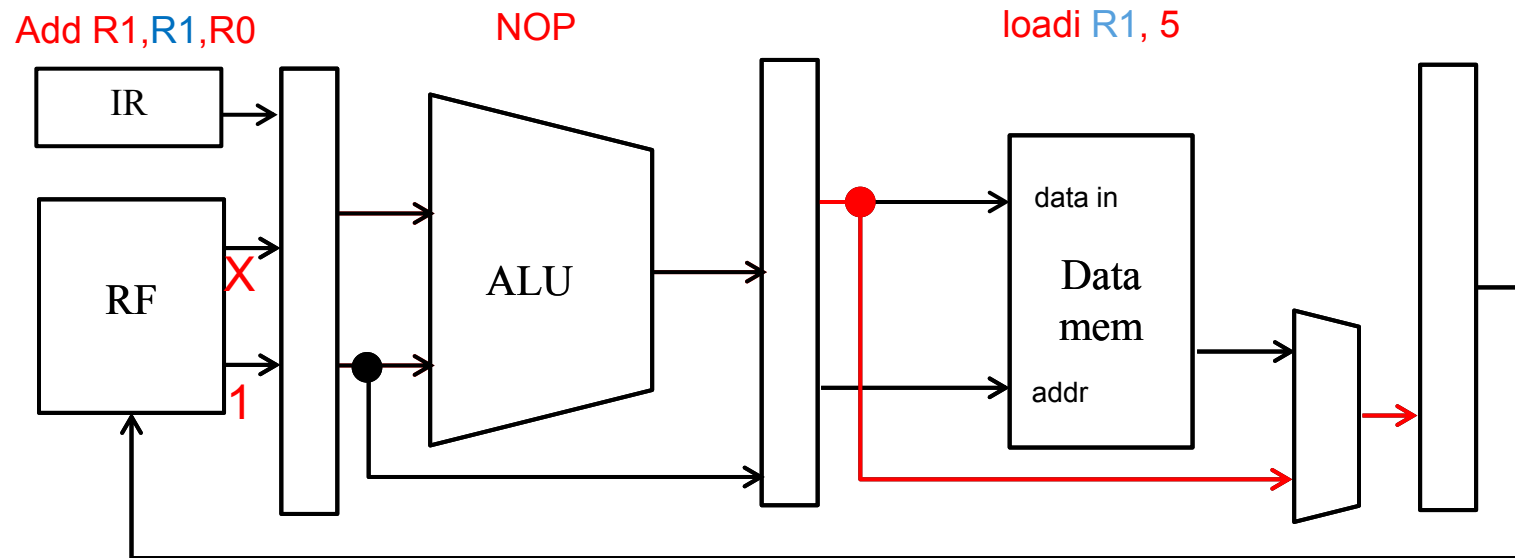 Data Hazard

loadi Rd, imm


opcode	Rd		immediate
0 1 1 0	b b b	x	b b b b b b b b



• First solution: Using NOPs

4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)

Data Hazard

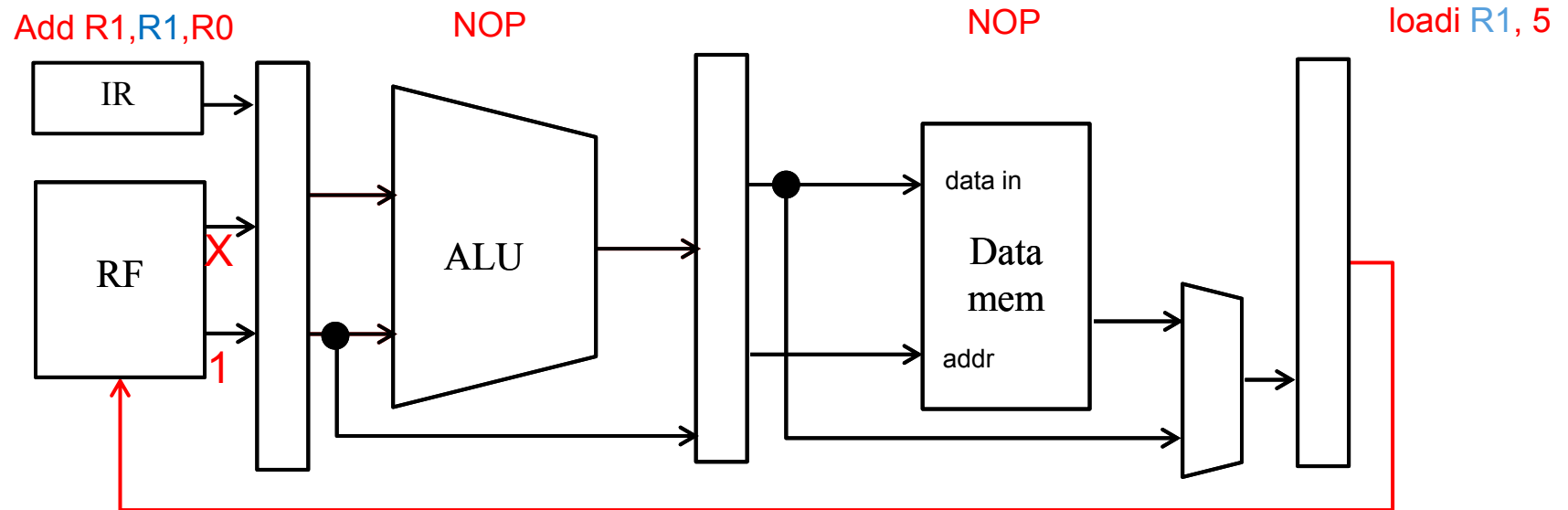

loadi Rd, imm


opcode	Rd		immediate
0 1 1 0	b b b	x	b b b b b b b b



• First solution: Using NOPs

4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)


Data Hazard

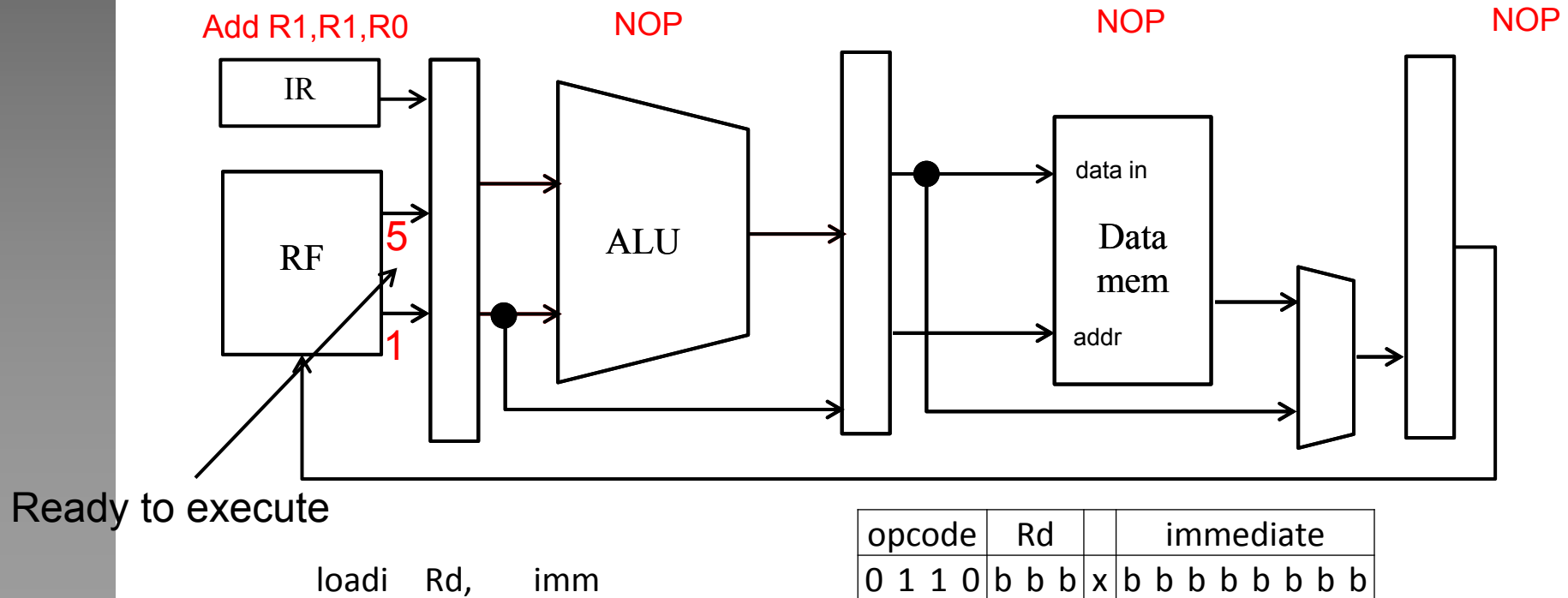



• Second solution: Data Forward

4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)

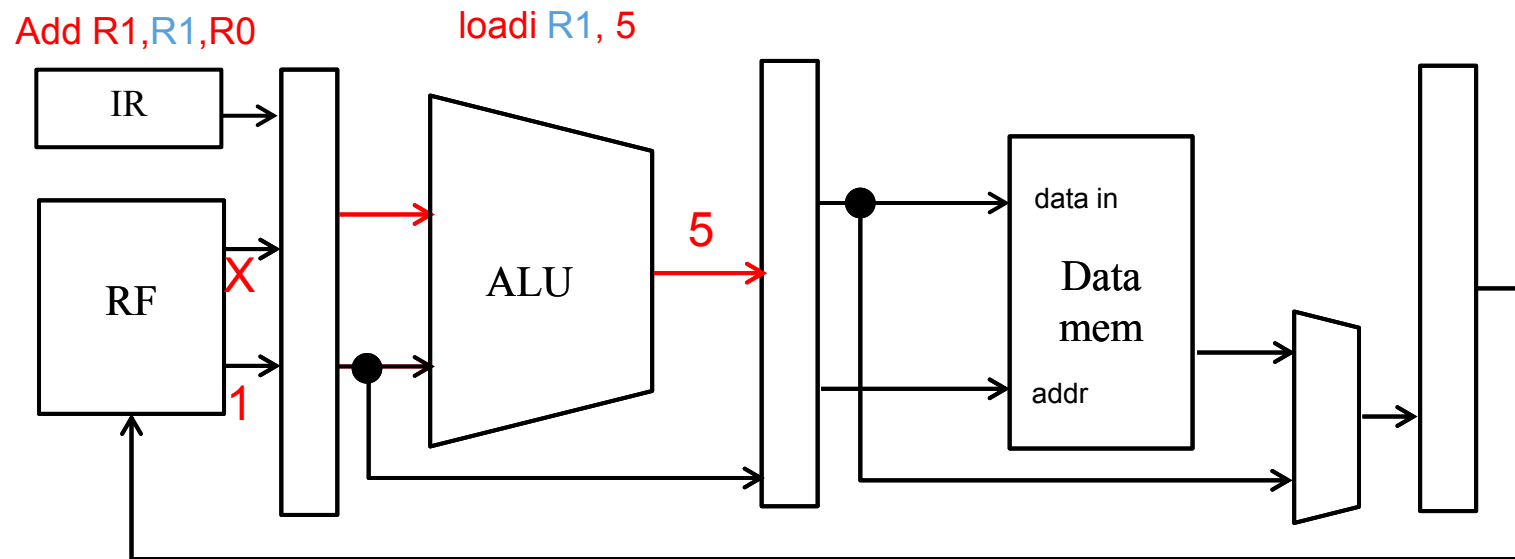 Data Hazard


loadi Rd, imm

opcode	Rd		immediate
0 1 1 0	b b b	x	b b b b b b b b



• Second solution: Data Forward

4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)

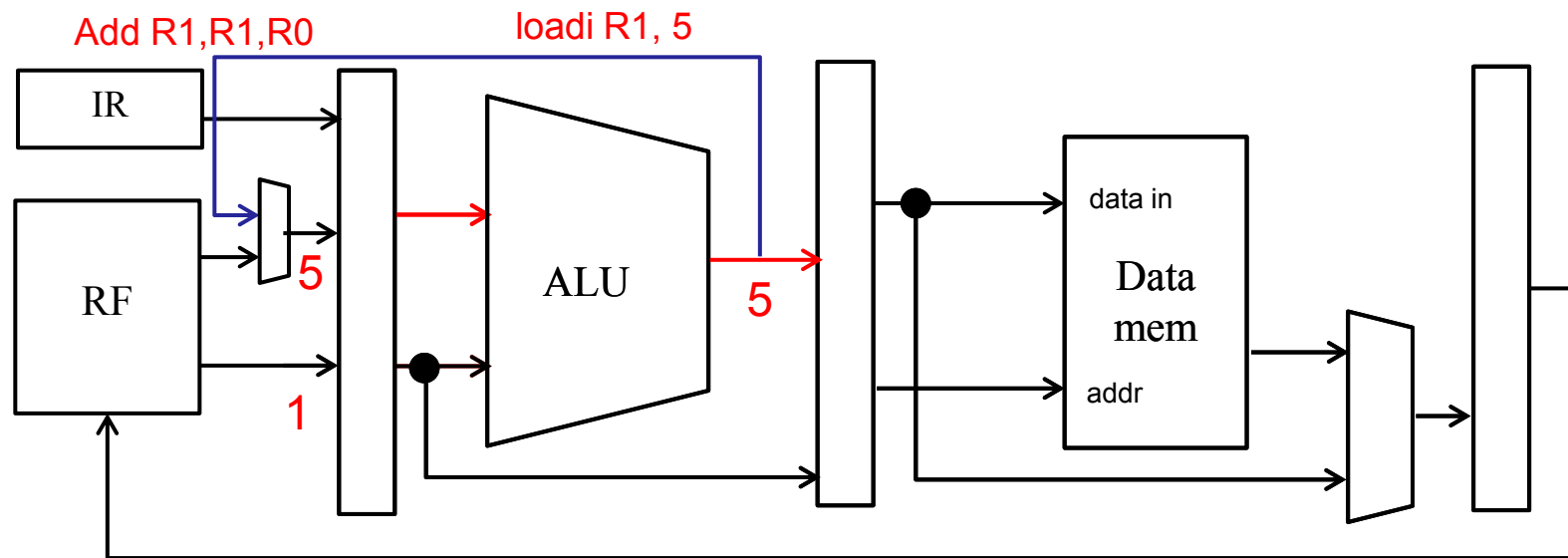 Data Hazard

loadi Rd, imm

opcode	Rd		immediate
0 1 1 0	b b b	x	b b b b b b b b



- How to solve this hazard?

0	input	R0	(R0 = input = 1)
1	loadi	R2, 8	(R2 = 8)
2	loadi	R6, 0	(R6 = 0)
3	loadi	R7, 50	(R7 = 50)
4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)
6	store	R1, @R7	(mem[50] = 6)
7	load	R5, @R7	(R5 = mem[50] = 6)
8	sub	R5, R5, R0	(R5 = R5 - 1)
9	brnz	R5, @R2	(if (R5 != 0) PC = 8)
10	loadi	R3, 255	(R3 = 255)
11	output	R3	(output = 255)

Data Hazard

Also solved with data forwarding!





- How to solve this hazard?

0	input	R0	(R0 = input = 1)
1	loadi	R2, 8	(R2 = 8)
2	loadi	R6, 0	(R6 = 0)
3	loadi	R7, 50	(R7 = 50)
4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)
6	store	R1, @R7	(mem[50] = 6)
7	load	R5, @R7	(R5 = mem[50] = 6)
8	sub	R5, R5, R0	(R5 = R5 - 1)
9	brnz	R5, @R2	(if (R5 != 0) PC = 8)
10	loadi	R3, 255	(R3 = 255)
11	output	R3	(output = 255)

Data Hazard

Can we solve this hazard with forwarding mechanism?






• Second solution: Data Forward

7	load	R5, @R7	(R5 = mem[50] = 6)
8	sub	R5, R5, R0	(R5 = R5 - 1)

Data Hazard

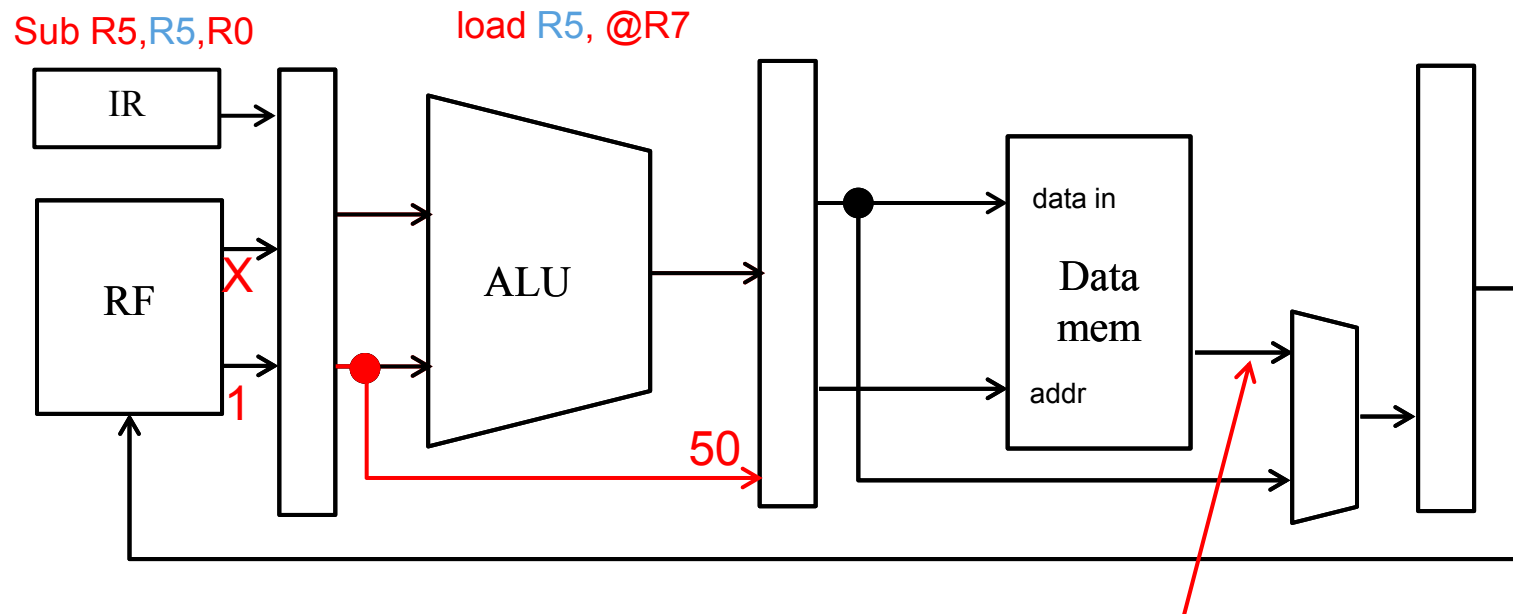

R5 is only available here!!! The pipeline has to be stalled



7	load	R5, @R7	(R5 = mem[50] = 6)
8	sub	R5, R5, R0	(R5 = R5 - 1)

Diagram illustrating the execution of the instruction `Sub R5, R5, R0` (labeled `NOP` in the diagram). The instruction is fetched from the IR (Instruction Register) and decoded. The RF (Register File) provides register indices. The ALU (Arithmetic Logic Unit) performs the subtraction operation. The Data Memory is accessed at address 50 to retrieve the value 6, which is then stored in register R5. The instruction is labeled `Sub R5, R5, R0` and `NOP`.



- How to solve this hazard?

0	input	R0	(R0 = input = 1)
1	loadi	R2, 8	(R2 = 8)
2	loadi	R6, 0	(R6 = 0)
3	loadi	R7, 50	(R7 = 50)
4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)
6	store	R1, @R7	(mem[50] = 6)
7	load	R5, @R7	(R5 = mem[50] = 6)
8	sub	R5, R5, R0	(R5 = R5 - 1)
9	brnz	R5, @R2	(if (R5 != 0) PC = 8)
10	loadi	R3, 255	(R3 = 255)
11	output	R3	(output = 255)

Data & Control Hazard





• How to solve this hazard?

```
8  sub    R5, R5, R0    (R5 = R5 - 1)
9  brnz   R5, @R2       (if (R5!=0) PC = 8)
10 loadi  R3, 255        (R3 = 255)
```

Control Hazard

PC	8	9	10	8	9
IR[15:0]	66ff	1b40	BRNZ	LOADI	SUB
Instruction[1]	0000	1b40	b0a8	0000	1b40
bubble	1				

When the BRNZ instruction is fetched, the PC already points to 10, so in the next posedge Clk, the LOADI will be fetched.

However the instruction that should be executed is the SUB instruction, since the jump condition is true


To solve this hazard a bubble is introduced





8	sub	R5, R5, R0	(R5 = R5 - 1)
9	brnz	R5, @R2	(if (R5 != 0) PC = 8)
10	loadi	R3, 255	(R3 = 255)


Control Hazard

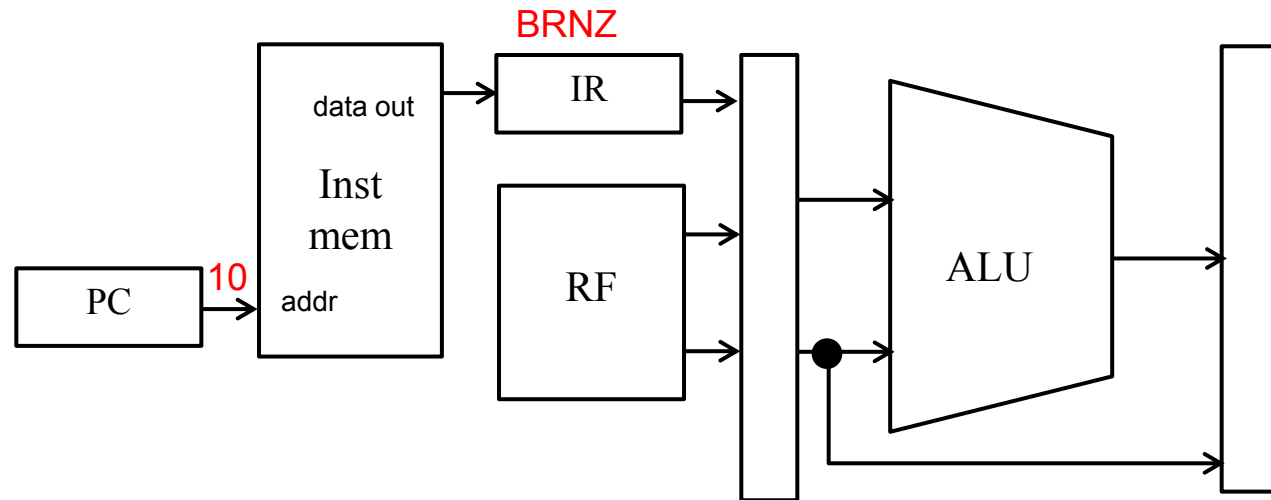




8	sub	R5, R5, R0	(R5 = R5 - 1)
9	brnz	R5, @R2	(if (R5 != 0) PC = 8)
10	loadi	R3, 255	(R3 = 255)

Control Hazard

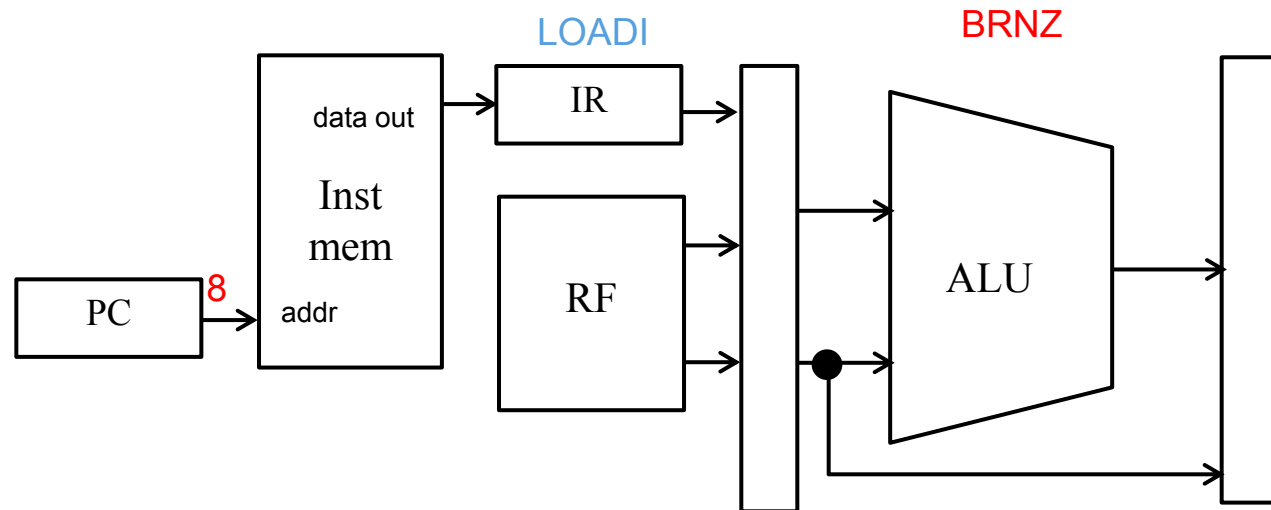



Control Hazard

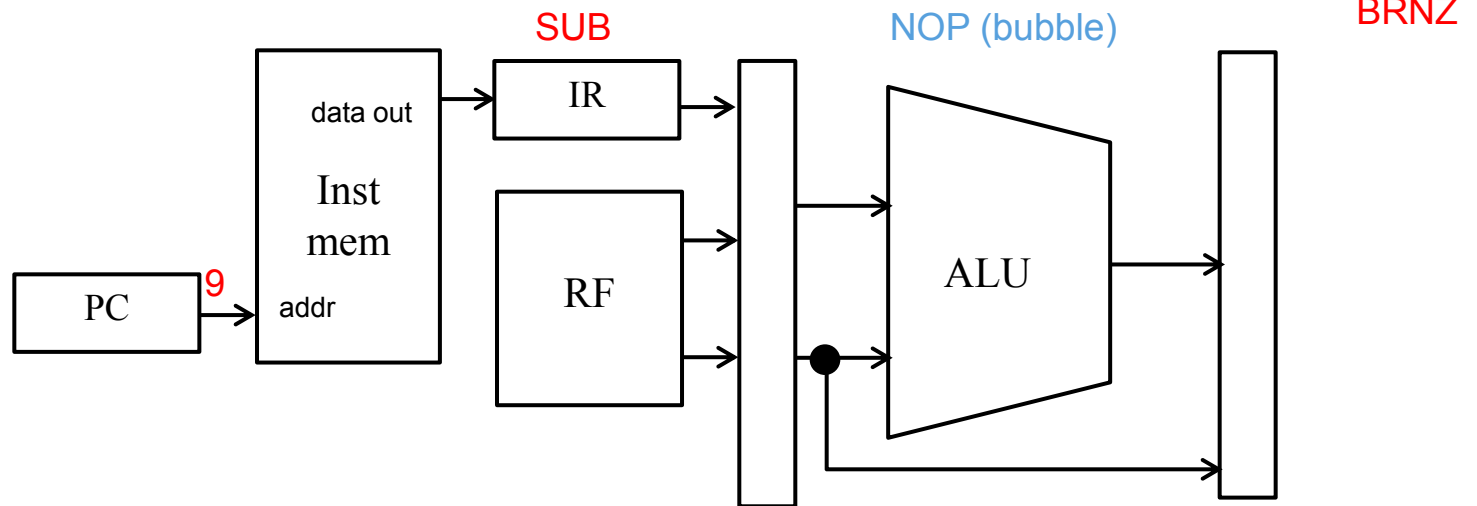



- How to solve this hazard?

0	input	R0	(R0 = input = 1)
1	loadi	R2, 8	(R2 = 8)
2	loadi	R6, 0	(R6 = 0)
3	loadi	R7, 50	(R7 = 50)
4	loadi	R1, 5	(R1 = 5)
5	add	R1, R1, R0	(R1 = 5 + 1 = 6)
6	store	R1, @R7	(mem[50] = 6)
7	load	R5, @R7	(R5 = mem[50] = 6)
8	sub	R5, R5, R0	(R5 = R5 - 1)
9	brnz	R5, @R2	(if (R5 != 0) PC = 8)
10	loadi	R3, 255	(R3 = 255)
11	output	R3	(output = 255)

Data Hazard

Also solved with data forwarding!





Results

- Pipeline without data forwarding executes this code in 605ns




Too many
NOPs



Results

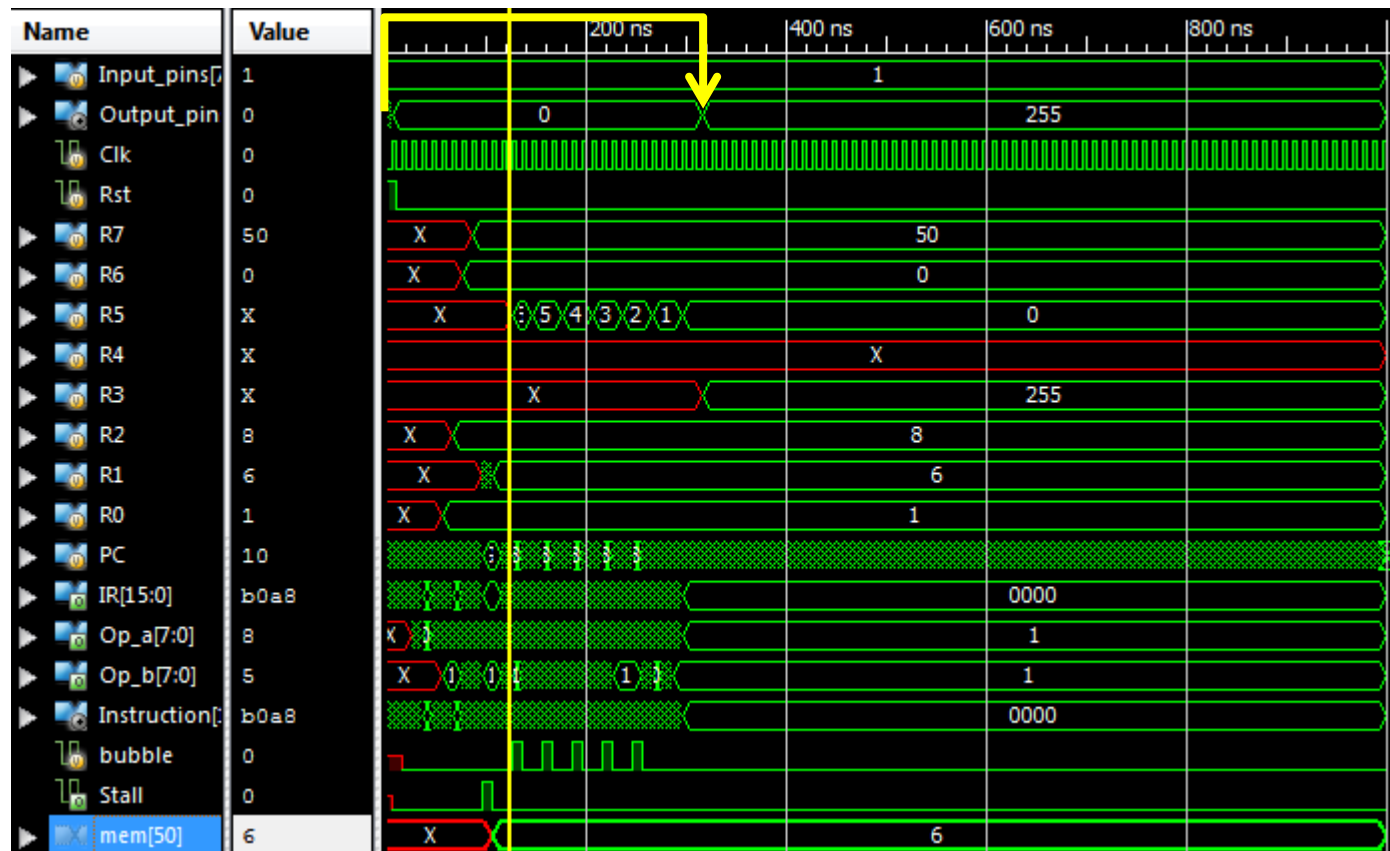- While the version with data forward implemented executes in 315ns (almost half of the time!)





Future work

- Extend the microprocessor
 - Add more instructions
 - Mov between Registers
 - MOV R3, R4
 - Other branch conditions
 - BRN, BRC
 - Halt
 - Stop execution
 - Add support to Jump and Link
- Develop Assembler





Embedded Systems
Research Group

- THE END

